

```
1  // Eugene Ngo
2  // 5/3/23
3  // EE 469
4  // Lab 3
5
6  // fullAdder takes in 2 bits, a and b, as well as a possible carry in bit and adds them
   together
7  // if there is a carry out, we output that bit in cout.
8  module fullAdder (A,B,cin,sum,cout);
9      input logic A,B,cin;
10     output logic sum,cout;
11
12     assign sum = A ^ B ^ cin;
13     assign cout = A & B | cin & (A^B);
14 endmodule
15
16 module fullAdder_testbench();
17     logic A,B,cin,sum,cout;
18     fullAdder dut (A,B,cin,sum,cout);
19
20     integer i;
21     initial begin
22         for (i = 0; i < 2**3; i++) begin
23             {A,B,cin} = i; #10;
24         end
25     end
26
27 endmodule
28
```